
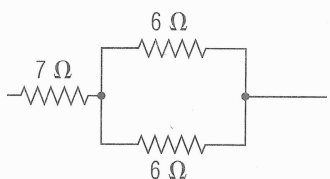


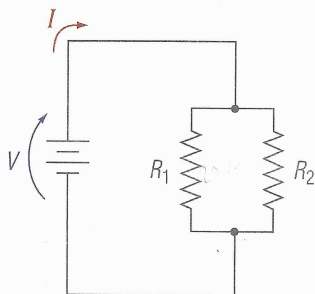
- 39. A current of 1.50×10^{-2} A flows through a 30.0Ω resistor. What is the voltage drop across the resistor?
- 40. A 1.50 V cell is connected to a 1.50Ω light bulb in a simple circuit. How much current flows through the bulb?
- 41. A 12.0 V battery produces a current of 1.00 mA when connected in a circuit to resistor R . What is R 's resistance?
- 42. A 55.0 W bulb is connected in a circuit to a voltage source of $V_{\max} = 110.$ V.
 - a. What current does it draw?
 - b. What is its resistance?
- 43. A 40.0Ω resistor in a circuit draws a current of 0.100 A.
 - a. What is the voltage drop across the resistor?
 - b. How much electrical power does it absorb?
- 44. Find the resistance of two $1.50 \times 10^3 \Omega$ resistors
 - a. in series.
 - b. in parallel.




- 46. In the figure below, $R_1 = R_2 = 20.0 \Omega$ and $V = 10.0$ V. Find I .




- 47. What is I in the figure below?

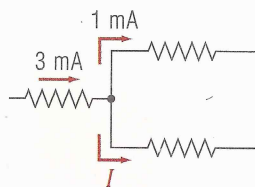

- 48. What is V in the figure below?

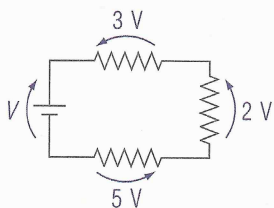


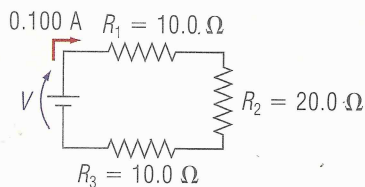- 49. a. Find the equivalent resistance of the circuit below.




- b. Find the voltage drop across R_1 .
- c. Find the voltage drop across R_2 .
- d. Find the voltage drop across R_3 .
- e. What is V ?

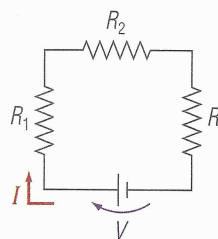- 50. The voltage drop across R_1 is 2.00 V. $R_1 = 20.0 \Omega$; $R_2 = 30.0 \Omega$; $V = 6.00$ V.




- a. What is the current through R_1 ?
- b. What is the current through R_3 ?
- c. What is the voltage drop across R_2 ?
- d. What is the total voltage drop in the circuit external to the voltage source?
- e. What is the voltage drop across R_3 ?
- f. What is R_3 ?

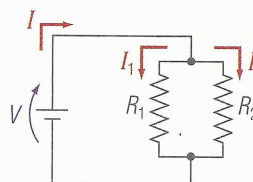- 51. $V = 6.00$ V; $R_1 = 30.0 \Omega$; $R_2 = 60.0 \Omega$.



- a. Find the equivalent resistance of the circuit.
- b. Find the total current I through the circuit.
- c. What is the voltage drop across R_1 ?
- d. What is the voltage drop across R_2 ?
- e. What is the current through R_1 ?
- f. What is the current through R_2 ?

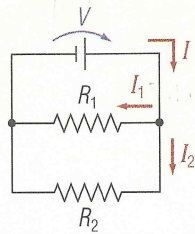52. $V = 10.0 \text{ V}$; $I_1 = 0.100 \text{ A}$; $I_2 = 0.0500 \text{ A}$.



- What is the voltage drop across R_1 ?
- What is the voltage drop across R_2 ?
- Calculate R_1 .
- Calculate R_2 .
- Calculate the circuit's equivalent resistance.
- Calculate the current through the voltage source.
- Compare R_1/R_2 with I_1/I_2 .

53. The resistor bridge in the figure below contains fixed resistors $R_1 = 10.0 \Omega$, $R_2 = 100.0 \Omega$, variable resistor R_3 , and unknown resistance R_x . Find R_x when the galvanometer (G) reads 0 A , and $R_3 = 50.0 \Omega$.

